



COLLEGE OF ENGINEERING SUNY POLYTECHNIC INSTITUTE

ECE 260

Name: _____

Date: _____

Laboratory 6 – Operational Amplifiers

Purpose: In this lab, you will design amplifiers based on the 741 integrated-circuit op-amp.

Equipment Required

- Breadboard and variable power supply
- FLUKE Hand-held Digital Multimeter (DMM)
- Various resistors
 - Two 1 k Ω resistors
 - 4.7 k Ω resistor

Learning Objectives


1. Discuss the purpose of an op-amp
2. Determine inverting and non-inverting circuit configurations
3. The effect of load resistances on an op-amp circuit

Theory

An operational amplifier (op-amp) is a device with two inputs and a single output. The output of the amplifier is given by $V_{out} = A (V_p - V_n)$, where A is the open-loop voltage gain (i.e. gain without feedback), V_p is the non-inverting input voltage, and V_n is the inverting input voltage. Typically, the open-loop voltage gain A is on the order of 10^3 to 10^6 .

One important feature of op-amps is that a resistor can be placed between the output node and the inverting input to provide feedback and adjust amplification. While operating in its linear region ($-V_{cc} < V_{out} < +V_{cc}$), the op-amp adjusts its output current such that the voltage difference between the two inputs is nearly zero (i.e. $V_p = V_n$). When the output swings to $V_{out} = \pm V_{cc}$, however the op-amp is operating in its saturation region, and it cannot balance V_p and V_n . Our general-purpose 741 op-amp requires two power supply voltages, ± 15 V, for normal operation.

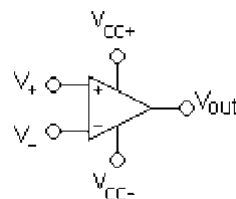The 741 op-amp is a bipolar-junction-transistor-based amplifier, has an input resistance of about 2 M Ω . Because of this high input resistance, only a very small current (on the order of a μ A) flows into either input of the op-amp and is essentially zero when we model it as an ideal op-amp (open-loop voltage gain A goes to infinity).



I_p = current flowing into V_+ (V_p)

I_n = current flowing into V_- (V_n)

Figure 1: An operational amplifier

Operational amplifier circuits

Non-Inverting Amplifier

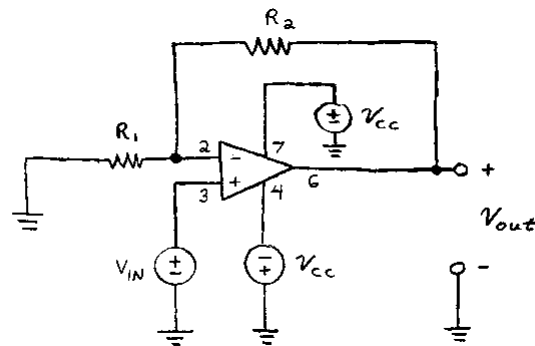


Figure 2 – Non-inverting Amplifier

The operational amplifier of Figure 2 is called a *non-inverting amplifier*. When a voltage is applied between the V_p terminal (pin 3) and ground, the op-amp output V_{out} (pin 6) will tend to become positive. This increase in voltage, which is measured relative to ground, is attenuated by the voltage divider formed by R_1 and R_2 and fed back to the op-amp's V_n terminal (pin 2), where it also appears as a voltage with respect to ground. The positive voltage applied between V_n and ground by V_{out} counteracts the increase in V_{out} by tending to force V_{out} in the negative direction. The output voltage will thus reach an equilibrium in which the voltage of the V_n terminal relative to ground rises to almost the same value as the voltage applied between the V_p terminal and ground. In this state, with $V_n = V_p$, and with $V_n = V_{out} (R_1 + R_2) / R_1$, the op-amp output becomes

$$V_{out} = V_{in} * (R_1 + R_2) / R_1$$

When V_{out} reaches the value in this equation, the V_n and V_p terminals acquire nearly the same voltage. This condition is sometimes called a *virtual short circuit*.

Inverting Amplifier

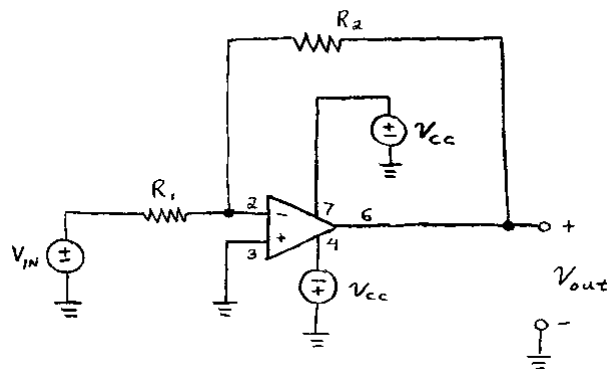


Figure 3 – Inverting Amplifier

The circuit of Figure 3 is called an *inverting amplifier*. The current flowing from V_{in} into R_1 must also flow through R_2 , because essentially zero current flows into the high resistance of the V_n terminal (pin 2) of the op-amp. When a V_{in} is applied, the output voltage of the op-amp adjusts itself until the voltage between V_n and V_p falls toward zero. With the V_p terminal (pin 3) grounded, the V_n terminal (pin 2) also remains at ground potential, causing all of V_{in} to appear across R_1 . The current flowing through R_1 determined by Ohm's Law, thus becomes $i_1 = V_{in}/R_1$. This same current must flow as i_2 through R_2 . With V_n at ground, the op-amp voltage becomes

$$V_{out} = -i_2 R_2 = -V_{in} * (R_2/R_1)$$

The factor $-R_2/R_1$ multiplying V_{in} is called the *gain* of the amplifier. This particular op-amp circuit has a negative gain. Positive increases in V_{in} lead to negative increases in V_{out} ; conversely, negative increases in V_{in} lead to positive increases in V_{out} . The op-amp responds to any voltage difference between its V_n and V_p terminals by increasing the magnitude of V_{out} .

Procedure

1. Non-inverting Amplifier with Given Resistors

- Obtain two resistors, $R_1 = 1 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$. Measure the values of these resistors and record their values in Table 1.
- Build the circuit of Figure 2 with a 741 op-amp and these resistors. Refer to the datasheet in the appendix for the op-amp pin diagram. (Note that V_{cc} is VEE on the datasheet.)
- Note: You'll need to place the op-amp across one of the gaps along a terminal strip such that you don't short any of the op-amp's pins together by placing them in the same row of 5 holes. Here is a checklist of the necessary connections for your circuit:
 - ⇒ R_1 to op-amp pin 2 and ground (one of the blue outer rails)
 - ⇒ op-amp pin 3 to variable power supply
 - ⇒ op-amp pin 4 to $-V_{cc}$ power supply (-15 or -12 V)
 - ⇒ op-amp pin 7 to $+V_{cc}$ power supply (+15 or +12 V)
 - ⇒ R_2 to op-amp pin 2 and op-amp pin 6
 - ⇒ ground bus to ground terminal of power supply
- Calculate the gain of this op-amp circuit (with your measured resistor values) and record in Table 1.

Table 1

Parameters	Calculated Values	Measured Values
R_1		
R_2		
Gain		

What do you expect the value of V_{out} for a given value of V_{in} ?

-
-
- Set the variable power supply, $V_{in} = 1\text{ V}$. Verify this value with the voltmeter (*always use verified values in your tables*).
 - Measure V_{out} (pin 6). Record this value. Calculate V_{out}/V_{in} and record this value as well.
 - Repeat for $V_{in} = 2\text{V}$, 4V , 8V , and 16V

Table 2

V_{in}	Measured Values		
	V_{in}	V_{out}	V_{out}/V_{in}
1			
2			
4			
8			
16			

Does the experimental gain (V_{out}/V_{in}) match the gain you calculated earlier, for all values of V_{in} ? Why or why not?

2. Non-inverting Amplifier Design

- Design a non-inverting amplifier with a gain of approximately 4. **Show how you determine the necessary resistor values.**
- Measure the required resistor values and record them in your notebook
- Build the circuit with a 741 op-amp and these resistors. (Again, note that V_{CC-} is V_{EE} on the data sheet).
- Apply +12V (or +15V) to V_{CC+} (pin 7) and -12V (or -15V) to V_{CC-} (pin 4).
- Set $V_{in} = 0.5V$. Verify this with a voltmeter (**always use verified values in your tables**).
- Measure V_{out} . Record this value in Table 3. Calculate V_{out}/V_{in} and record this value as well.
- Repeat for $V_{in} = 1V, 1.5V, 2V, 3V$.

Table 3

V_{in}	Measured Values		
	V_{in}	V_{out}	V_{out}/V_{in}
0.5			
1.00			
1.50			
2.00			
3.00			

Does the experimental gain (V_{out}/V_{in}) match your desired gain, for all values of V_{in} ? Why or why not?

3. Inverting Amplifier with Given Resistors

- Obtain two resistors, $R_1 = 1.2 \text{ k}\Omega$ and $R_2 = 5 \text{ k}\Omega$. Measure the values of these resistors and record their values in Table 4.
- Build the circuit of Figure 3 with a 741 op-amp and these resistors. Refer to the datasheet in the appendix for the op-amp pin diagram.
- Calculate the gain of this op-amp circuit (with your measured resistor values) and record in Table 4.

Table 4

Parameters	Calculated Values	Measured Values
R_1		
R_2		
Gain		

What do you expect the value of V_{out} for a given value of V_{in} ?

- Set the variable power supply, $V_{in} = 1 \text{ V}$. Verify this value with the voltmeter.
- Measure V_{out} . Record this value in Table 5. Calculate V_{out}/V_{in} and record this value as well.
- Repeat for $V_{in} = 1.5\text{V}$, 2V , 2.5V , and 3V

Table 5

V_{in}	Measured Values		
	V_{in}	V_{out}	V_{out}/V_{in}
1			
1.5			
2			
2.5			
3			

Does the experimental gain (V_{out}/V_{in}) match the gain you calculated earlier, for all values of V_{in} ? Why or why not?

4. Inverting Amplifier Design

- Design an inverting amplifier with a gain of approximately -1. **Show how you determine the necessary resistor values.**
- Measure the required resistor values and record them in your notebook
- Build the circuit with a 741 op-amp and these resistors. (Again, note that V_{cc-} is V_{EE} on the data sheet).
- Apply +12V to V_{cc+} (pin 7) and -12V to V_{cc-} (pin 4).
- Set $V_{in} = 0.5V$. Verify this with a voltmeter (**always use verified values in your tables**).
- Measure V_{out} . Record this value in Table 6. Calculate V_{out}/V_{in} and record this value as well.
- Repeat for $V_{in} = 1.5V, 2.5V, 3.5V, 4.5V$.


Table 6

V_{in}	Measured Values		
	V_{in}	V_{out}	V_{out}/V_{in}
0.5			
1.5			
2.5			
3.5			
4.5			

Does the experimental gain (V_{out}/V_{in}) match your desired gain, for all values of V_{in} ? Why or why not?

5. Inverting Amplifier with a Load Resistor

- Redraw figure 3 with a load resistor

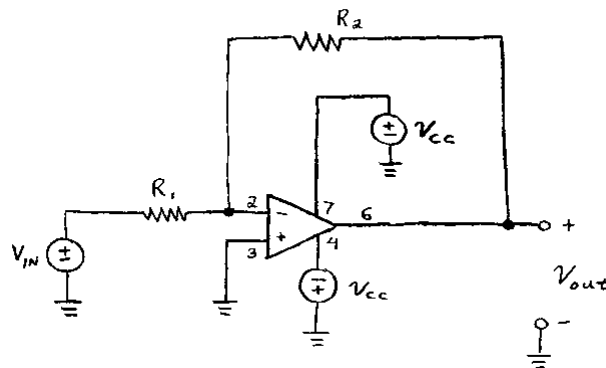

- Determine V_{out} as a function of V_{in} . Show this derivation in the notes.

Is this equation you used to derive V_{out} different from the equation derived for an amplifier circuit without a load? Why or why not?

Using the inverter circuit you designed in part 4...

- Obtain a 4.7 k Ω resistor. Measure and record its value.

Table 7

Parameters	Calculated Value	Measured Value
R_{load}		

- Connect this resistor between the op-amp output (V_{out}) and the ground bus (be sure the ground bus is connected to ground on your power supply).
- Apply +12V to V_{cc+} (pin 7) and -12V to V_{cc-} (pin 4).
- Set $V_{in} = 0.5V$. Verify this with a voltmeter (*always use verified values in your tables*).
- Measure V_{out} . Record this value in Table 8. Calculate V_{out}/V_{in} and record this value as well.
- Repeat for $V_{in} = 1.5V, 2.5V, 3.5V, 4.5V$.

Table 8

V_{in}	Measured Values		
	V_{in}	V_{out}	V_{out}/V_{in}
0.5			
1.5			
2.5			
3.5			
4.5			

Does the load resistor affect the gain of the amplifier? Why is this useful?

6. Operational Amplifier Non-Idealities

What is the voltage difference $V_p - V_n$ for an ideal op-amp? Record your results in Table 9.

What are the input currents (I_p and I_n) for an ideal op-amp? Record your results in Table 9.

Using the same inverting amplifier circuit from Part 5...

- Measure the voltage difference between V_p and V_n (pins 3 and 2). Record this value in Table 9.

Does this voltage reading match your answer above? Why or why not?

- Measure the currents flowing into these op-amps (I_p and I_n). Record these values in Table 9. *Be careful not to blow the fuse in the multimeter!!*

Do these current readings match your answer above? Why or why not?

Table 9


Parameter	Expected Value	Measured Value
$V_+ - V_-$		
I_+		
I_-		

Questions:


(1) Why do we need V_{cc} ? What is its function?

(2) When does an op-amp operate within its *linear* region? When does an op-amp operate in its *saturation* regions?

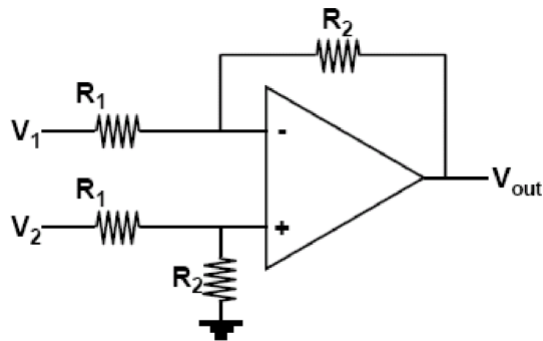
(3) What is the purpose of the following circuit? (Determine V_{out} as a function of V_1 , V_2 , R_1 , and R_2 .)



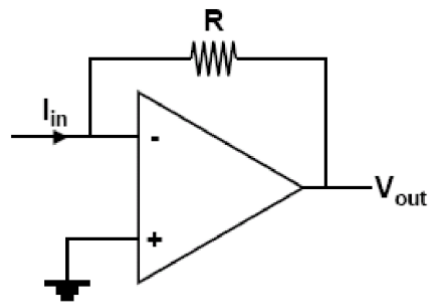(4) What is the purpose of the following circuit? (Hint: What is the *input* to the “system” and what is the *output* of the “system”?)



NON-INVERTING AMPLIFIER

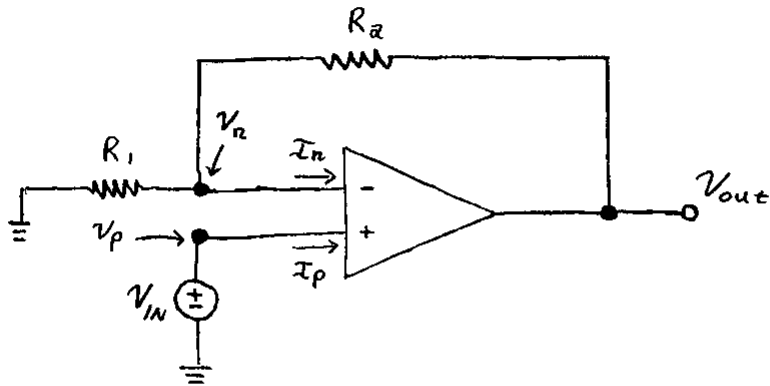

ideal characteristics : $I_n = I_p = 0$

$$V_n = V_p$$

KCL @ node V_n : $\frac{V_n - 0}{R_1} + \frac{V_n - V_{out}}{R_2} = 0$

@ node V_p , $V_p = V_{IN}$


$$\therefore \frac{V_{IN}}{R_1} + \frac{V_{IN} - V_{out}}{R_2} = 0$$

$$R_2 V_{IN} + R_1 (V_{IN} - V_{out}) = 0$$

$$R_2 V_{IN} + R_1 V_{IN} = R_1 V_{out}$$

$$\boxed{\frac{V_{out}}{V_{IN}} = \frac{R_2 + R_1}{R_1}}$$

INVERTING AMPLIFIER

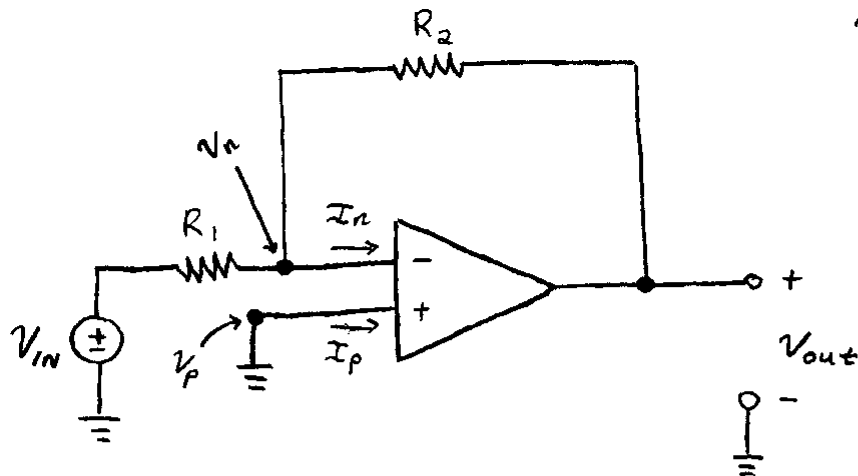

ideal characteristics : $I_p = I_n = 0$
 $V_p = V_n$

$$\text{KCL @ node } V_n : \frac{V_n - V_{IN}}{R_1} + \frac{V_n - V_{out}}{R_2} = 0$$

$$\text{@ node } V_p : V_p = 0$$

$$\therefore \frac{0 - V_{IN}}{R_1} + \frac{0 - V_{out}}{R_2} = 0$$

$$-R_2 V_{IN} = R_1 V_{out}$$

$$\boxed{\frac{V_{out}}{V_{IN}} = \frac{-R_2}{R_1}}$$

NOTES

HA17741/PS

General-Purpose Operational Amplifier
(Frequency Compensated)

HITACHI

ADE-204-043 (Z)

Rev. 0

Dec. 2000

Description

The HA17741/PS is an internal phase compensation high-performance operational amplifier, that is appropriate for use in a wide range of applications in the test and control fields.

Features

- High voltage gain : 106 dB (Typ)
- Wide output amplitude : ± 13 V (Typ) (at $R_L \geq 2$ k Ω)
- Shorted output protection
- Adjustable offset voltage
- Internal phase compensation

Ordering Information

Application	Type No.	Package
Industrial use	HA17741PS	DP-8
Commercial use	HA17741	

Pin Arrangement

